


A division of PhIE Learning Center

GATE ECE and EE Coaching by IITians GATE CLASSES

Networks and Circuits

CHAPTER 1 – BASIC ELECTRONICS

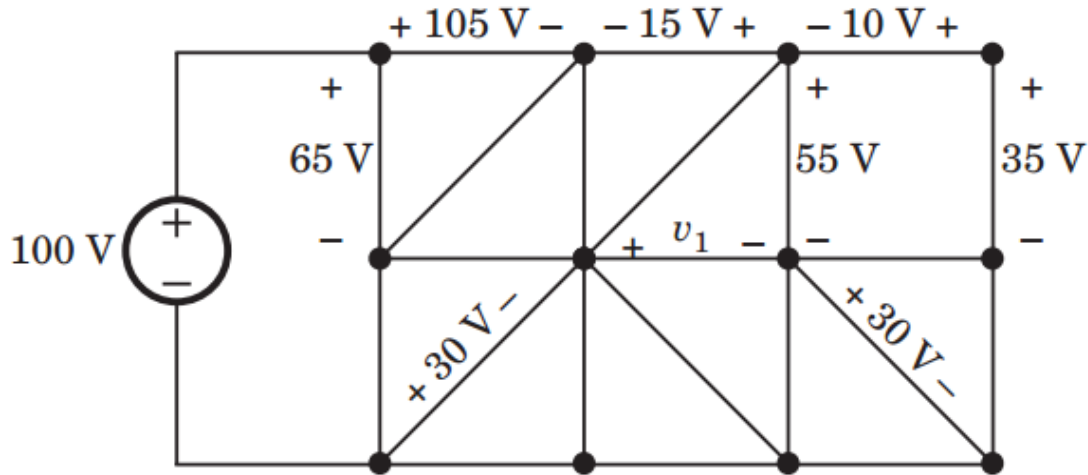
Q.1. Consider the circuit graph shown in fig. Each branch of circuit graph represent a circuit element. The value of voltage v_1 is



(A) 30 V	(B) 25 V
(C) 20 V	(D) 15 V

ANS (D)


Q.2. R_{eq} ?

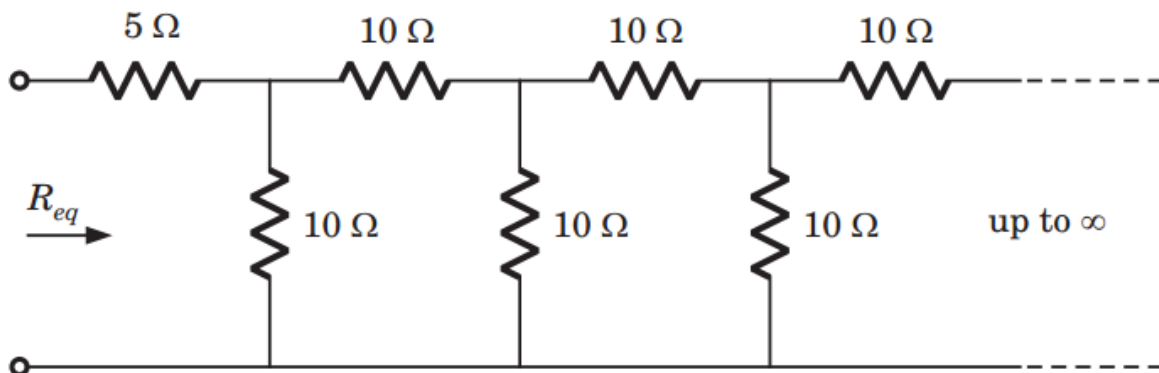

- | | |
|---------------------|---------------------|
| (A) $11.86\ \Omega$ | (B) $10\ \Omega$ |
| (C) $25\ \Omega$ | (D) $11.18\ \Omega$ |

ANS (D)

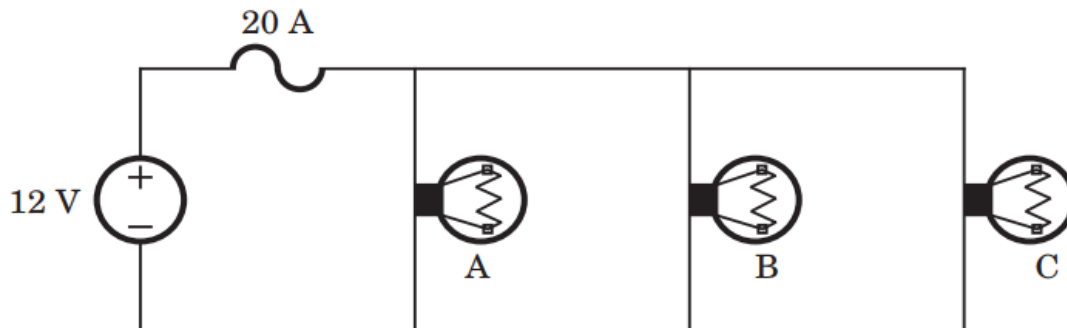
Q.3. In the circuit of fig. bulb A uses 36 W when lit, bulb B uses 24 W when lit, and bulb C uses 14.4 W when lit. The additional A bulbs in parallel to this circuit, that would be required to blow the fuse is



- (A) 4 (B) 5
(C) 6 (D) 7

ANS (B)

Q.4. C_{eq} ?

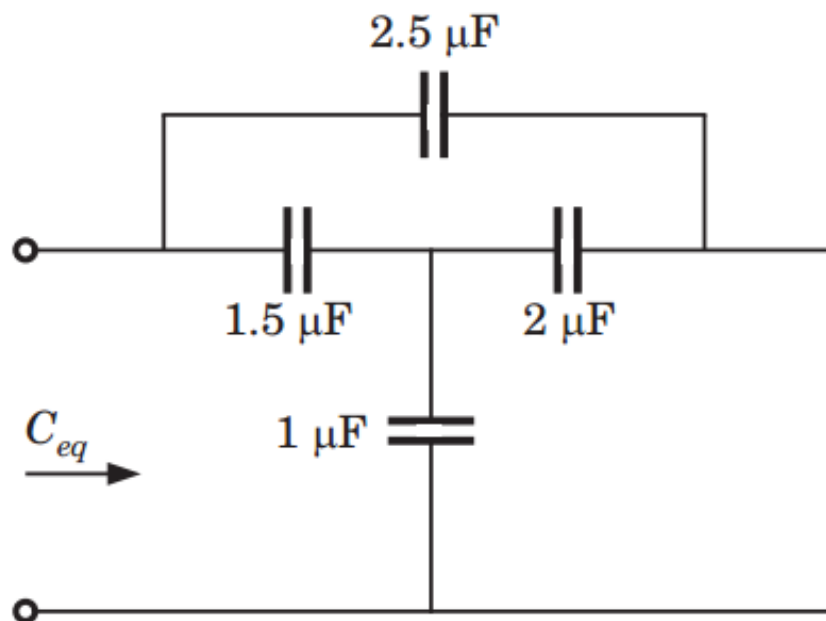

- | | |
|-----------|-----------|
| (A) 3.5 F | (B) 1.2 F |
|-----------|-----------|




A division of PhIE Learning Center

(C) 2.4 F	(D) 2.6 F
-----------	-----------

ANS (A)

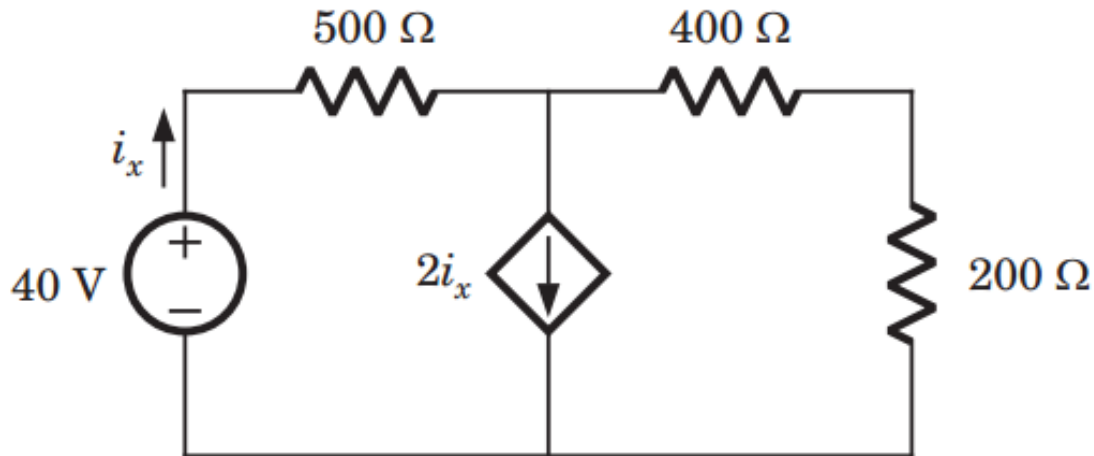Q.5. In the circuit of fig. power is delivered by



- (A) dependent source of 192 W
- (B) dependent source of 368 W
- (C) independent source of 16 W
- (D) independent source of 40 W

ANS (A)

Q.6. The waveform for the current in a 200 F capacitor is shown in fig. The waveform for the capacitor voltage is



A division of PhIE Learning Center



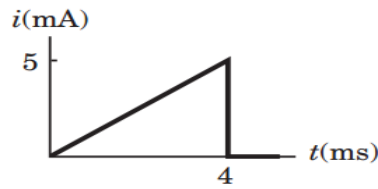



Fig. P. 1.1.36

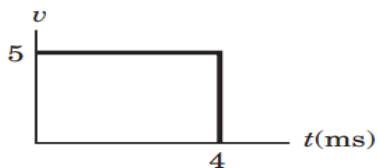


(A)

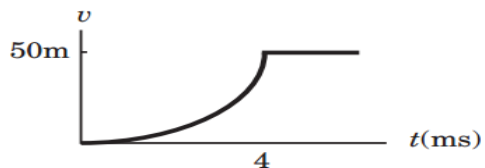

(B)

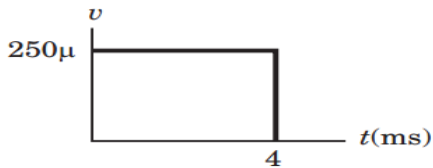


(C)

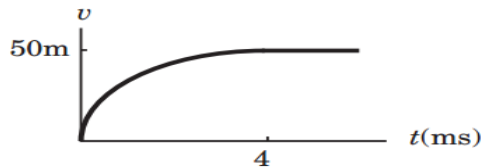

(D)

ANS (B)

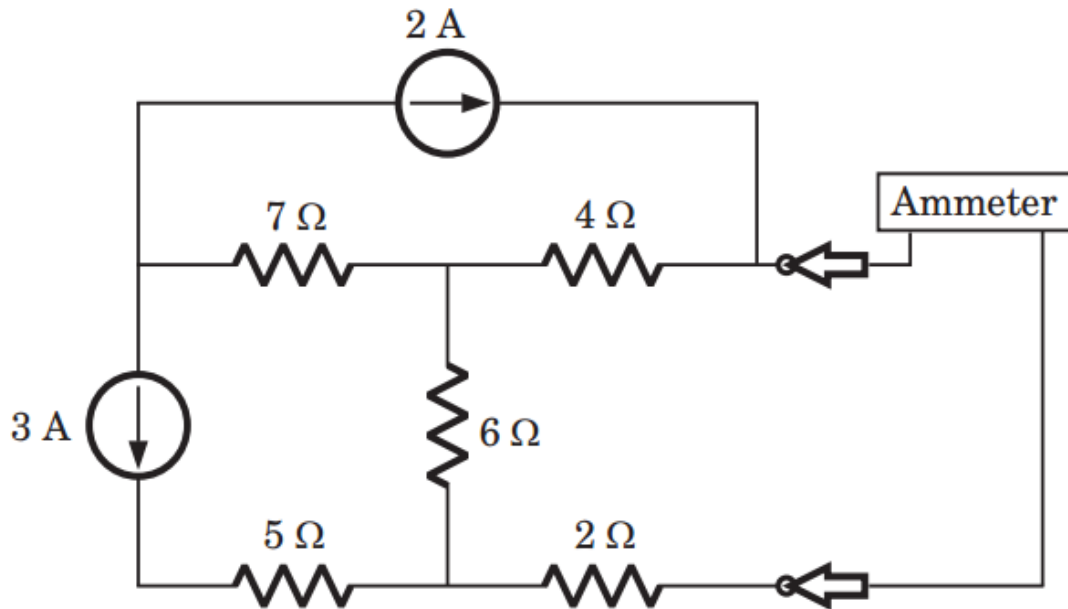Q.7. The value of the current measured by the ammeter in Fig is




A division of PhIE Learning Center

- (A) $\frac{2}{3}$ A (B) $\frac{5}{3}$ A
(C) $-\frac{5}{6}$ A (D) $\frac{2}{9}$ A

ANS (C)

Q.8. V_a ?

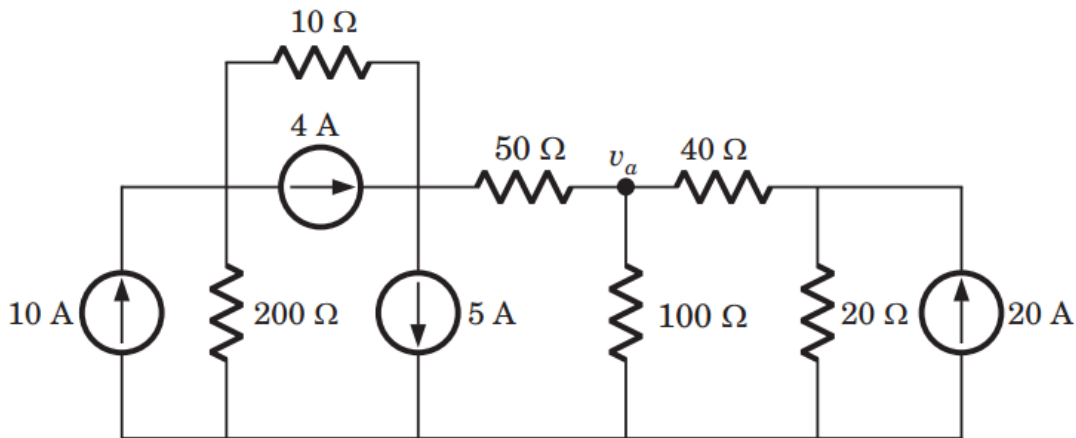


- (A) 342 V (B) 171 V
(C) 198 V (D) 396 V

ANS (A)

Q.9. The power being dissipated in the 2Ω resistor in the circuit of Fig. is



A division of PhIE Learning Center

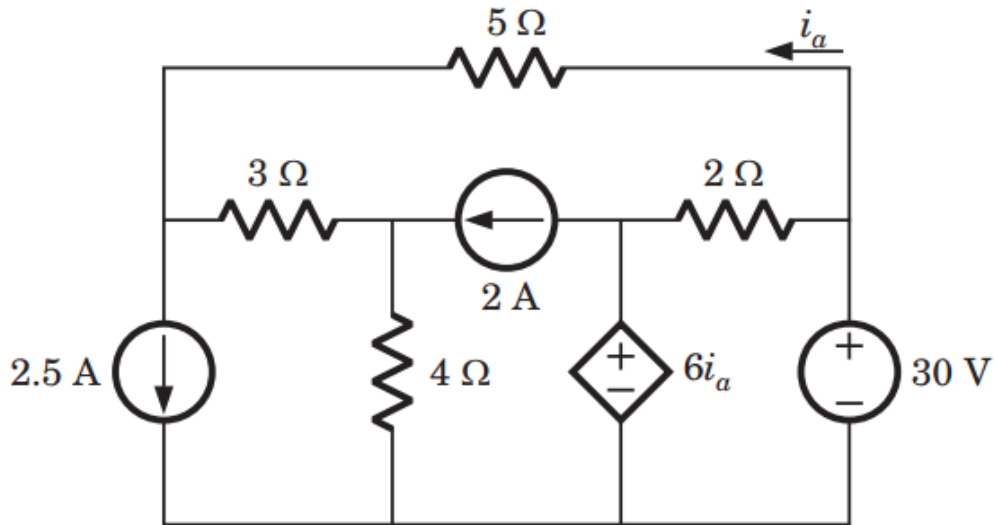

- (A) 76.4 W (B) 305.6 W
(C) 52.5 W (D) 210.0 W

ANS (A)

Q.10 R_{eq} ?

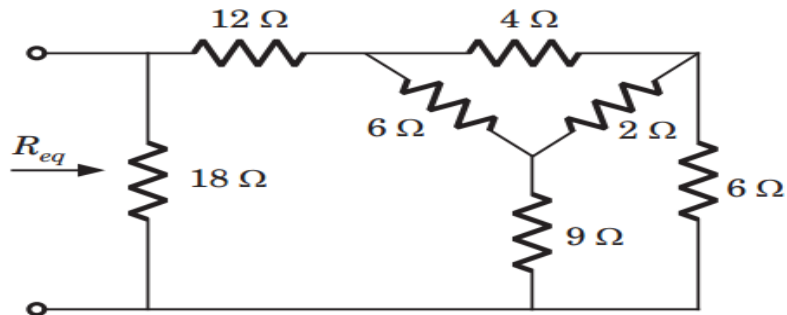


Fig. P.1.4.30


- (A) 18Ω (B) $\frac{72}{13} \Omega$
(C) $\frac{36}{13} \Omega$ (D) 9Ω

ANS (D)

Q. 11. In the circuit shown, the power supplied by the voltage source is




A division of PhIE Learning Center

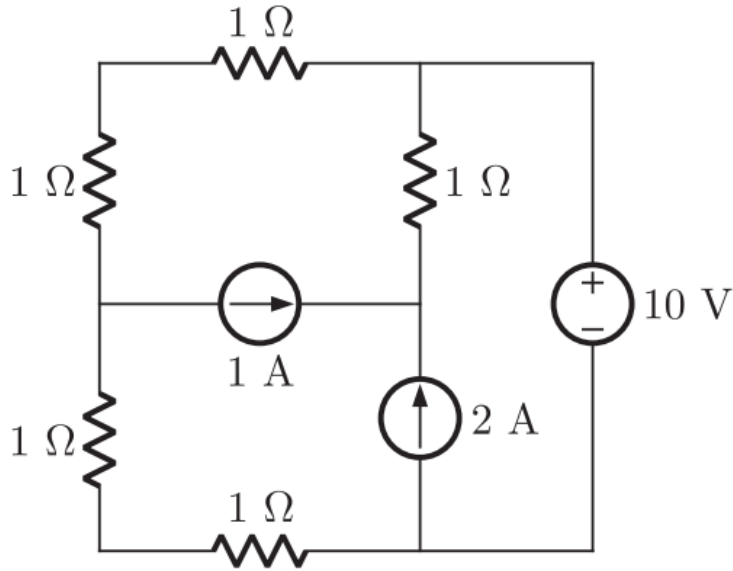

- (A) 0 W (B) 5 W
 (C) 10 W (D) 100 W

ANS (A)

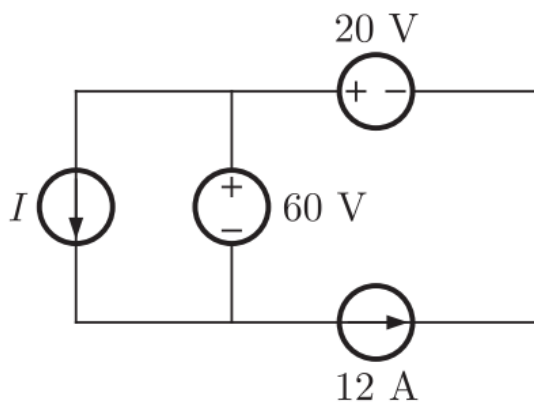Q.12. In the interconnection of ideal sources shown in the figure, it is known that the 60 V source is absorbing power.



Which of the following can be the value of the current source I ?


- | | |
|----------|----------|
| (A) 10 A | (B) 13 A |
| (C) 15 A | (D) 18 A |

ANS (A)



A division of PhIE Learning Center

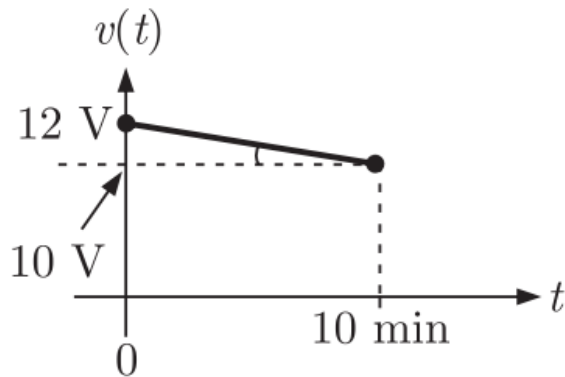
Q. 13. A fully charged mobile phone with a 12 V battery is good for a 10 minute talk-time. Assume that, during the talk-time the battery delivers a constant current of 2 A and its voltage drops linearly from 12 V to 10 V as shown in the figure. How much energy does the battery deliver during this talk-time?



- (A) 220 J (B) 12 kJ
(C) 13.2 kJ (D) 14.4 J

ANS (C)

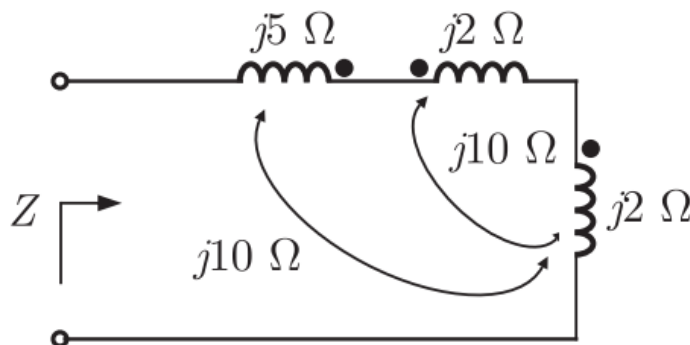Q. 14. Impedance Z as shown in the given figure is




- | | |
|-----------------|-----------------|
| (A) $j29\Omega$ | (B) $j9\Omega$ |
| (C) $j19\Omega$ | (D) $j39\Omega$ |

ANS (B)



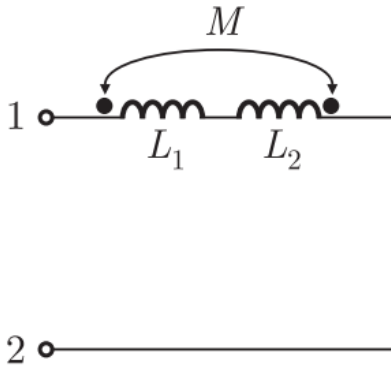Q.15 The equivalent inductance measured between the terminals 1 and 2 for the circuit shown in the figure is



(A) $L_1 + L_2 + M$

(B) $L_1 + L_2 - M$

(C) $L_1 + L_2 + 2M$

(D) $L_1 + L_2 - 2M$

ANS (D)

Q.16 If each branch of Delta circuit has impedance $\sqrt{3} Z$, then each branch of the equivalent Wye circuit has impedance

(A) $Z/\sqrt{3}$ (B) $3Z$

(C) $3\sqrt{3} Z$ (D) $Z/3$

ANS (A)

